

DAY - 18

SEAT NUMBER

--	--	--	--	--	--

2020	III	13	1100	V - 267	(E)
ELECTRONICS PAPER - II (C-2)					
Time : 3 Hours		4 Pages		Max. Marks : 50	

- Instructions :** (1) All questions are compulsory.
(2) Draw neat labelled diagrams wherever necessary.
(3) Figures to the right indicate full marks.
(4) Use of log tables is allowed.

1. (A) Select correct alternatives from the following sub-questions and rewrite the complete sentences :

- (a) The radix of decimal number system is _____ 1
- (i) 2
(ii) 8
(iii) 10
(iv) 16
- (b) The bubbled OR gate is equivalent to _____ gate. 1
- (i) NAND
(ii) NOR
(iii) NOT
(iv) AND
- (c) In _____ analog to digital converter SAR is used. 1
- (i) Simultaneous
(ii) Counter
(iii) Successive Approximation
(iv) Continuous

- (d) _____ memory improve the overall performance of a computer. 1
- (i) Magnetic Core
 - (ii) Cache
 - (iii) Magnetic Tape
 - (iv) Floppy Disk

(B) Attempt **any two** of the following :

- (a) What is a full Adder ? Explain its working with logic diagram and truth table. 3
- (b) Explain the working of 1:4 Demultiplexer with logic diagram. 3
- (c) How many Flip-flops are required to construct each of the following counters : 3
 - (i) MOD - 10 Counter
 - (ii) MOD - 20 Counter
 - (iii) MOD - 100 Counter

2. (A) Attempt **any two** of the following :

- (a) Convert the following : 3
 - (i) $[11001.101]_2 = [\text{---}]_{10}$
 - (ii) $[10111]_2 = [\text{---}]_{10}$
 - (iii) $[2AF]_{16} = [\text{---}]_2$
- (b) Implement the following logic expression using Multiplexer. 3
 $f(A, B, C, D) = \sum m (1,2,5,8,9,13,15)$
- (c) Write comparison between Primary Memory and Secondary Memory. 3

(B) Attempt **any one** of the following :

- (a) Draw the block diagram of Mod-16 counter and explain its working with truth table. 4
- (b) Draw the block diagram of Digital Computer. And explain the function of each block. 4

3. (A) Attempt **any two** of the following :
- (a) Perform the following subtraction of Binary number's using 2's complement method : 3
- (i) $11011 - 10100$
- (ii) $1010 - 1110$
- (b) What is 'T' Flip-flop ? Why it is known as 'divide by 2 circuit' ? 3
- (c) What will be the output voltage of 4-bit R-2R ladder type DAC corresponding to the binary inputs : 3
- (i) 1000
- (ii) 0100
- Given Logic '0' = 0V
Logic '1' = 10V
- (B) Attempt **any one** of the following :
- (a) State and prove De-morgan's theorems. Draw logic diagram. 4
- (b) Explain working of decimal to BCD Encoder by using 4-OR gates with the help of circuit diagram.
4. (A) Attempt **any two** of the following :
- (a) Write a note on BCD Code. State its advantages and disadvantages 3
- (b) Explain basic gates with their definition, truth table and symbols. 3
- (c) With a neat circuit diagram, explain, how will you use IC 7446 as a BCD to seven Segment Decoder in drive seven segment LED display ? 3
- (B) Attempt **any one** of the following :
- (a) Draw the circuit of TTL NAND gate and explain its working. Give importance of totem pole stage. 4
- (b) Explain the working of master - slave JK Flip-flop. 4
5. (A) Attempt **any two** of the following :
- (a) Define : 3
- (i) Power Dissipation
- (ii) Fan In and Fan Out
- (iii) Figure of Merit
- (b) Explain the working of BCD to Decimal decoder. 3
- (c) Explain clear and preset facility in Flip-flop. 3

(B) Attempt **any one** of the following :

- (a) What do you mean by : 4
- (i) LSB
 - (ii) MSB
 - (iii) Nibble
 - (iv) Byte
- (b) What is Multiplexer ? Obtain 8:1 multiplexer using two 4:1 multiplexer. 4

OR

5. (A) Attempt **any two** of the following :

- (a) Explain the basic CKT of CMOS Inverter. 3
- (b) What is Parallel Counter (Synchronous) ? Write its two advantages. 3
- (c) Explain the working of Successive approximation A/D converter. 3

(B) Attempt **any one** of the following :

- (a) Prove the following identities using boolean laws : 4
- (i) $ABC + A\bar{B}C + AB\bar{C} = A(B + C)$
 - (ii) $(A + B)(A + C) = A + BC$
- (b) Explain the working of Weighted Resistor DAC ? State its drawbacks. 4